## SEMESTER - 6 Comprehensive Lesson Plan: Digital and Analog Circuits and Instrumentation DSE-1B

#### **Overall Learning Objectives:**

- Understand the fundamental concepts of digital circuits and their applications.
- Analyze and design basic digital circuits using Boolean algebra and logic gates.
- Gain knowledge of semiconductor devices and their operation principles.
- Design and analyze basic transistor amplifier circuits.
- Understand the characteristics and applications of operational amplifiers.
- Apply operational amplifiers to perform various circuit functions.
- Get familiar with basic electronic instruments and their functionalities.
- Design and analyze power supply circuits and voltage regulation techniques.
- Understand the operation and applications of timer integrated circuits. Materials and Resources:
- Textbook: Digital Electronics by Morris Mano or similar resource.
- Lecture slides and handouts.
- Breadboard kits with electronic components (resistors, capacitors, diodes, transistors, integrated circuits).
- Function generators, oscilloscopes, multimeters (for laboratory sessions).
- Computer with simulation software (optional).
  - Assessment/Evaluation:
- Quizzes and assignments throughout the course to assess understanding of concepts.
- Midterm exam covering Units 1 and 2.

- Final exam covering all units.
- Laboratory reports documenting experiments and results.
- Project (optional): Design and build a simple digital circuit or application.
  Differentiation:
- Provide additional practice problems and explanations for struggling students.
- Offer challenging projects and in-depth explorations for advanced learners.
- Encourage group work and peer learning to benefit from diverse learning styles.

#### Lecture Schedule: <u>Unit 1: Digital Circuits (18 Lectures)</u>

- Learning Objectives:
- Differentiate between analog and digital signals.
- Understand binary number system and conversions.
- Analyze the operation of basic logic gates (AND, OR, NOT).
- Implement logic gates using diodes and transistors (optional).
- Apply De Morgan's theorems and Boolean algebra for logic simplification.
- Design combinational circuits using sum-of-products and Karnaugh maps.
- Perform binary addition, subtraction using 2's complement method.
- Analyze the operation of half adders, full adders, and subtractors.
- Design multi-bit adders and subtractor circuits.
- Activities:
- Interactive demonstrations of analog and digital signals.
- Binary number system conversions (practice problems).
- Logic gate truth table analysis and circuit simulations (using software or breadboard).
- $_{\circ}$   $\,$  De Morgan's theorem proofs and application exercises.
- Boolean algebra simplification problems (practice worksheets).
- Combinational circuit design using Karnaugh maps (hands-on exercises).

- Binary addition and subtraction by hand and using circuits.
- Design and analysis of multi-bit adder/subtractor circuits (assignments).

### **Unit 2: Semiconductor Devices and Amplifiers (24 Lectures)**

- Learning Objectives:
- Understand the operation principles of p-n junctions and diodes.
- Analyze diode characteristics (forward and reverse bias).
- Explain the working of LEDs, photodiodes, and solar cells.
- Understand the structure and characteristics of bipolar junction transistors (BJTs).
- Analyze BJT operation in common base (CB), common emitter (CE), and common collector (CC) configurations.
- Design transistor biasing circuits using voltage dividers.
- Analyze single-stage CE amplifier circuits using h-parameter equivalent model.
- Calculate amplifier parameters like gain, impedance, and power.
- Differentiate between Class A, B, and C amplifier operation.
- Activities:
- Demonstrations and simulations of p-n junction formation and diode behavior.
- Analysis of diode I-V characteristics and applications (practice problems).
- Explanation of LED, photodiode, and solar cell functionalities (presentations).
- BJT structure and characteristic curve analysis (interactive lectures).
- Biasing circuits design and simulations for BJT amplifiers.
- Hands-on laboratory experiments with BJTs and transistor testers (if available).
- Analysis of single-stage CE amplifier circuits using h-parameters (assignments).
- Design projects for different amplifier classes (optional).

### **Unit 3: Operational Amplifiers (12 Lectures)**

- Learning Objectives:
- Understand the ideal and practical characteristics of operational amplifiers.

- Analyze the concepts of open-loop and closed-loop gain.
- Explain the principle of virtual ground in Op-Amp circuits.
- Design and analyze inverting and non-inverting amplifier circuits.
- Apply Op-Amps for basic mathematical operations (addition, subtraction).
- Design integrator and differentiator circuits using Op-Amps.
- Understand the functionality of a zero-crossing detector circuit.
- Activities:
- Lecture and Discussion:
- Ideal and practical Op-Amp characteristics.
- Open-loop and closed-loop gain analysis.
- Concept of virtual ground and its implications.
- Derivation of gain equations for inverting and non-inverting amplifiers.
- Problem-Solving:
- Design and analyze inverting and non-inverting amplifier circuits for given specifications.
- Calculate the output voltage for different input signals.
- Design adder, subtractor, integrator, and differentiator circuits.
- Simulation (Optional):
- Simulate Op-Amp circuits using software like LTspice or Multisim to verify theoretical calculations.
- Laboratory Experiment (if available):
- Build and test basic Op-Amp circuits (inverting, non-inverting, adder) on a breadboard.

## **Unit 4: Instrumentation (13 Lectures)**

- Learning Objectives:
- Understand the basic principles of operation of a Cathode Ray Oscilloscope (CRO).
- Use a CRO to measure voltage, current, frequency, and phase difference.

- Understand the operation of different types of rectifiers (half-wave, full-wave).
- Analyze the performance of rectifier circuits (ripple factor, rectification efficiency).
- Understand the concept of filtering and its importance in power supplies.
- Understand the operation of Zener diodes and their use in voltage regulation.
- Understand the operation of the 555 timer IC in astable and monostable configurations.
- Activities:
- Lecture and Demonstration:
- Introduction to CRO: Block diagram, basic operation, controls.
- Half-wave and full-wave rectifier circuits: Analysis and waveforms.
- Capacitor filtering: Ripple factor calculations.
- Zener diode characteristics and voltage regulator circuits.
- 555 timer IC: Pin diagram, astable and monostable configurations.
- Laboratory Experiments:
- Use a CRO to measure voltage, current, frequency, and phase difference.
- Build and test half-wave and full-wave rectifier circuits.
- Design and implement a simple power supply with filtering.
- Experiment with 555 timer IC to generate different waveforms (square wave, pulse).

# **Unit 5: Sinusoidal Oscillators (5 Lectures)**

- Learning Objectives:
- Understand the concept of self-sustained oscillations.
- Understand Barkhausen's criterion for oscillation.
- Analyze the operation of RC oscillators (e.g., phase-shift oscillator, Wien bridge oscillator).
- Activities:
- Lecture and Discussion:
- Barkhausen's criterion for oscillation.

- Analysis of RC oscillator circuits (phase-shift oscillator, Wien bridge oscillator).
- Simulation (Optional):
- Simulate RC oscillator circuits using simulation software. Closure:
- Review and Summary:
- Review key concepts covered in the course.
- Conduct a comprehensive review session.
- Final Exam:
- Assess student understanding of all topics covered in the course.
- Include theoretical questions, problem-solving, and design-related questions.
  Note: